

Tutorial - 03

$S_1 \xrightarrow{\text{ON}} \text{OFF}$, $S_2 \xrightarrow{\text{ON}} \text{OFF}$

G E


Date _____

No. _____

- (a) A bulb in a staircase has two switches, one switch being at the ground floor and the other one at the first floor. The bulb can be turned ON and can be turned OFF and one of the switches irrespective of the state of the other switch.


S_1, S_2
↑
G ↓ FF

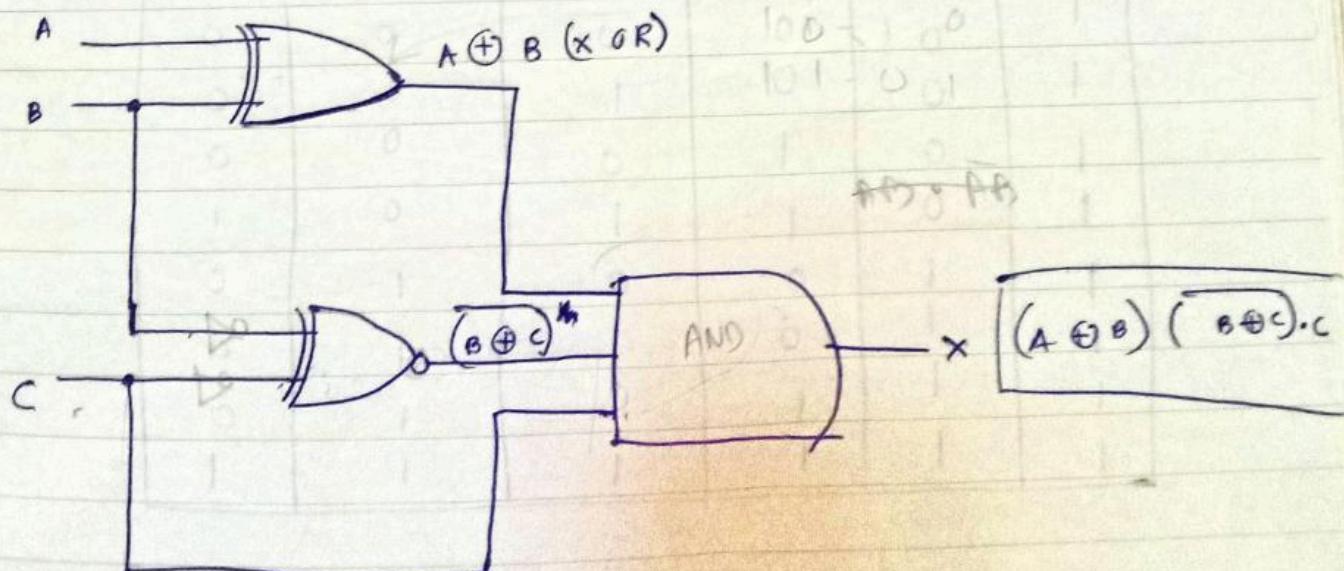- (b) Draw the truth table for above situation
- (b) Draw the most suitable logic circuit / gate for this
- (c) The Boolean function $Y = AB + CD$ is to be realized using only 2 input NAND gates.
- (a) Extract the Boolean function for NAND gates using the above formula.
- (b) Draw the logic circuit for the extracted Boolean function.
- (c) What is the Boolean expression for the given logic circuit below?



Answers

$s_1(a)$	$s_2(F)$	out put
0	0	0
0	1	1
1	0	1
1	1	0

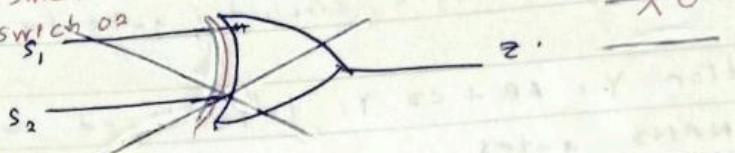 s_1 = switch 01 s_2 = switch 02rows of $2^2 = 4$ on adds and on minus
add = add on off odd

$$2^2 = 4$$

$$2^3 = 8$$

$$2^4 = 16$$

A	B	C	D	AB	CD
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	0	1
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	0	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	1
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	1	1

(b) P Q C D




(c)



	0	1	2	3
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	1	0	1

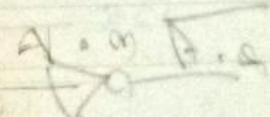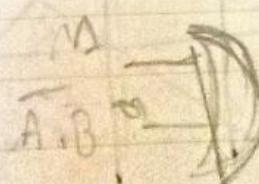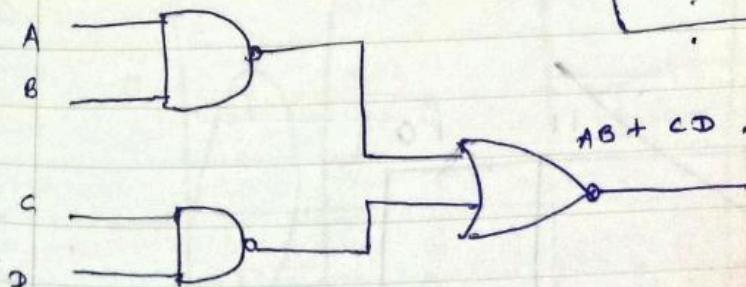(2) $y = AB + CD \Leftrightarrow y = \overline{A} \cdot \overline{B} + \overline{C} \cdot \overline{D}$

$$y = \overline{(AB)} \cdot \overline{(CD)}$$



Date _____
Pg. _____

De-Morgan's Law


$$(\overline{x+y}) = \overline{x} \cdot \overline{y}$$

$$\overline{x \cdot y} = (\overline{x} + \overline{y})$$

$$Y = AB + CD$$

$$= \overline{\overline{AB+CD}}$$

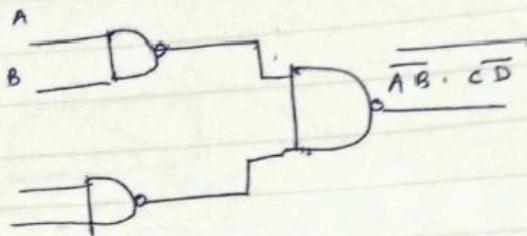
$$= \overline{\overline{AB} \cdot \overline{CD}}$$




26 / 05 / 2023

①


A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

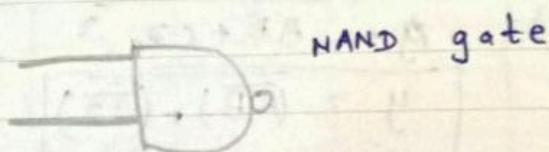

NAND gate

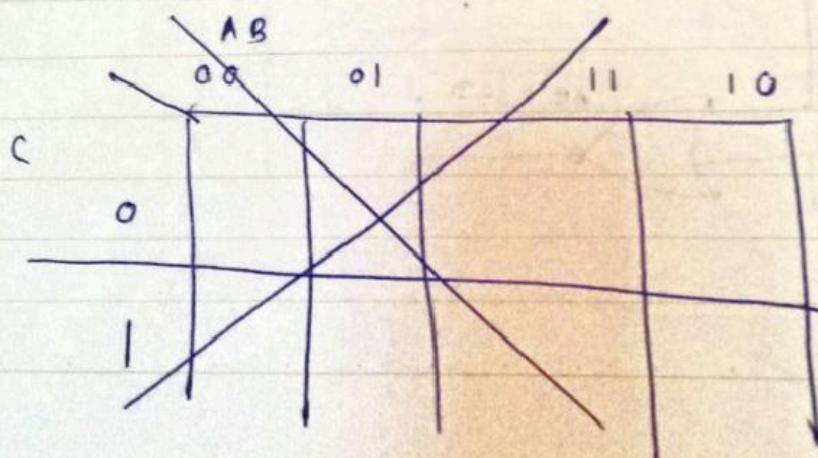

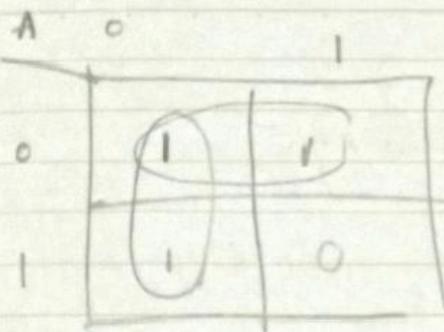
$$F = \bar{A}\bar{B} + \bar{A}B + A\bar{B}$$



$$\underline{F = \bar{B} + \bar{A}}$$

Q)

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

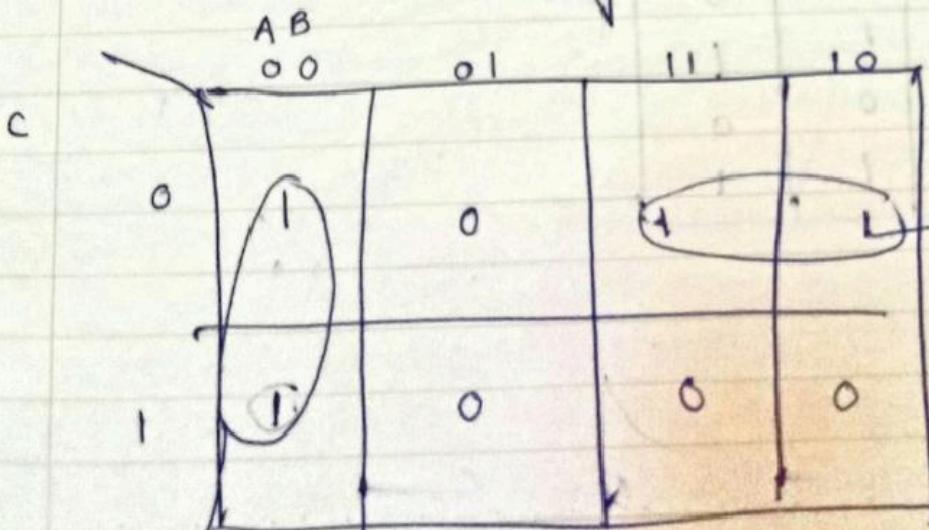

$$1 \Rightarrow A\bar{B}\bar{C} \\ 1 \Rightarrow A\bar{B}C \Rightarrow$$

$$AC$$

$$1 = \bar{A}\bar{B}\bar{C} \\ 1 = \bar{A}\bar{B}C \Rightarrow F = \bar{A}\bar{B}$$

$$F = \underline{\overline{AB}} + \underline{\overline{AC}}$$

$$F = \overline{ABC} + \overline{A}\overline{B}C + A\overline{B}C + ABC\overline{C}$$

on 27.2.

③

	A	B	C	D	out
0	0	0	0	0	0
0	0	0	0	1	1
0	0	0	0	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	1	1
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	1	1
1	0	1	0	1	1
1	1	0	0	0	0
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	1	1	1

$$\rightarrow F = \overline{ABC}\overline{D} + \overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D}$$


$$+ A\overline{B}C\overline{D} + \overline{A}\overline{B}C\overline{D} + ABC\overline{D}$$

$$+ ABC\overline{D}$$

exhibit 1. 3rd group to
411 @ 1032

in this exhibit add 319

312,3 group union
313 & 314

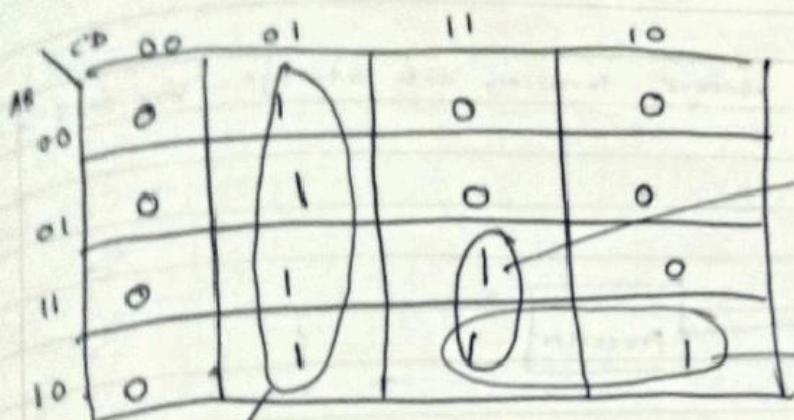

$$1 \Rightarrow \bar{C}DAB$$

$$1 \Rightarrow \bar{C}DAB\bar{B}$$

$$\bar{C}DA$$

$$1 \Rightarrow \bar{C}DAB\bar{B}$$

$$1 \Rightarrow \bar{C}\bar{D}AB\bar{B}$$

$$CA$$

$$1 \Rightarrow \bar{C}D\bar{A}\bar{B}$$

$$1 \Rightarrow \bar{C}D\bar{A}B$$

$$1 \Rightarrow \bar{C}DAB$$

$$1 \Rightarrow \bar{C}DAB\bar{B}$$

$$\Rightarrow \bar{C}D$$

$$F = \underline{\bar{C}D + CA + C\bar{D}A}$$


Register - To data storage • Temporary data storage. Very fast but small inside the CPU



delay \Rightarrow latency

Key - characteristics, (Register).

(1) speed \uparrow (nano seconds).

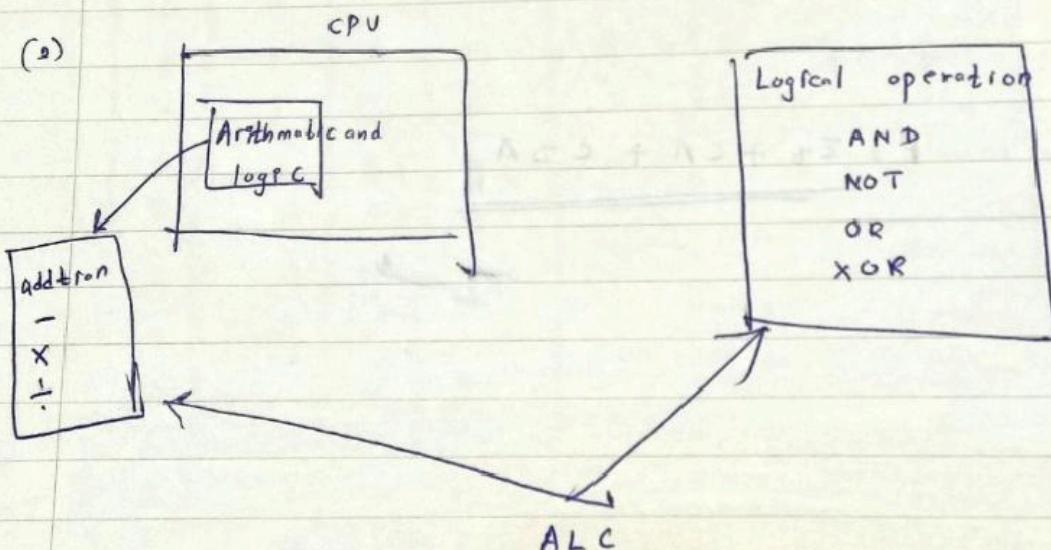

Arithmetic and logical expressions.

(2) small


(3) 8 - 64 bit store.

(4) 32 - 64 normal register, bits


(5) Registers

Purpose

main purpose data storing

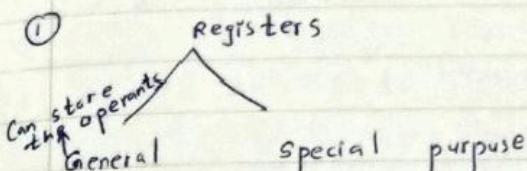

Use to operands.

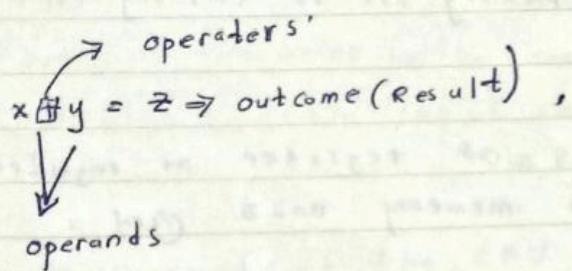

General

* Intermediate result produced

* $\text{int count} = 0;$
 loop parameters

* $\text{function parameter int } x \text{ or } y,$

2] stored,

Special purpose

designated task,

specific functions, (CPU and operations control).

* Program counters, (address of the current execution),

* Stack registers, (They manage the stack),

(3) What is the typical range of sizes for registers in a computer system?

(c) ~~32 to 64 bits~~

(4) How do registers contribute to the performance of a computer system?

- * By storing intermediate results during arithmetic operations.
- b) By minimizing the impact of memory latency.

(5) Which component of the CPU contains registers?

* Arithmetic logic unit (ALU).

(6) What is the purpose of general-purpose registers in computer architecture, and how are they typically used?

- * used for either memory address or data whenever needed.


(7) How does the program counter register contribute to the execution of a program in a CPU?

lecture
noteBasic Electricity And Diodes


Date _____

No. _____

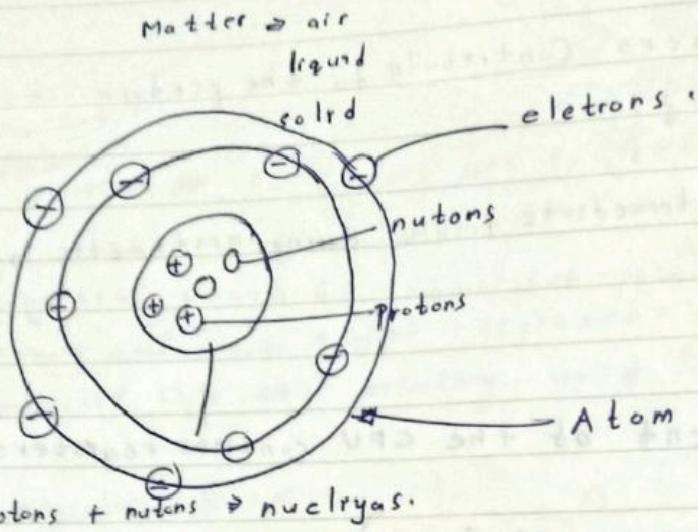Matter - basic unit of matter
has mass and app occupied space



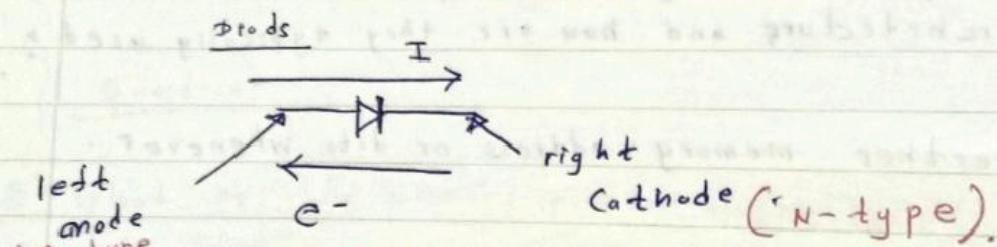electricity \Rightarrow is a form of energy !




Circuit diagram of a diode. It has \Rightarrow of go to one direction.
but electrons goes to opposite side

Common terms

- ① V is voltage (Volts: V);
voltage electrical potential difference between two points in a circuit
- ② I is current (amps: A);
The rate of flow of electric charge through a conductor.
- ③ R is resistance (ohms: Ω);
Resistance is the opposition to the flow of electric current in circuit.
- ④ C is capacitance (farads: F);
The ability of a capacitor to store and electric current.
When a voltage is applied
- ⑤ P is power (watt: W)
Power is the rate at which energy is transferred in an electrical circuit.

Electric Current

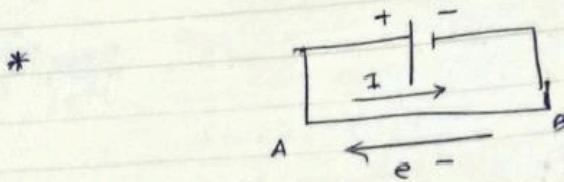

$$I \rightarrow + C$$

- * electric current is the "rate of flow of electric charges".
- 2. The unit used to measure the "charge" is Coulomb (C)
- 3. One coulomb of negative charge is the charge of 6.24×10^{18} electrons.
- 4. rate of flow - one coulomb per second is called, $\frac{1C}{\text{seconds}}$ = A.

Potential difference (V) = $\frac{\text{Work done (J)}}{\text{charge (c)}}$

$$V = \frac{1J}{1C}$$

Ohm's Law

$$\boxed{V = IR}$$

$$\frac{V}{R} = I$$

$$\frac{V}{I} = R$$

Power

$$\boxed{P = IV}$$

$$P = IV$$

$$P = \frac{V}{R} \times V$$

$$= I \times IR$$

$$P = \frac{V^2}{R}$$

$$\underline{\underline{P = I^2 R}}$$

(a) A circuit has a resistance of 10 ohms and current of 2 amperes, what is the voltage across the circuit.

$$R = 10$$

$$A =$$

$$I = R$$

$$V = IR$$

$$= 10 \times 2$$

$$= \underline{\underline{20 \text{ V}}}$$

(b) If a power supply provides a voltage of 12 volts and the circuit has a resistance of 4 ohms, what is the current flowing through the circuit?

$$* V = 12$$

$$R = 4$$

$$V = IR$$

$$\frac{V}{R} = I$$

$$\checkmark \frac{12}{4} = I$$

$$\underline{\underline{3 \text{ A} = I}}$$

(c) A light bulb has a resistance of 50 ohms and operates at a voltage of 120 volts. How much current does it draw?

$$* R = 50$$

$$V = 120$$

$$V = IR$$

$$\frac{V}{R} = I$$

$$\checkmark \frac{120}{50} = I$$

$$\underline{\underline{2.5 \text{ A} = I}}$$

- Date _____
④ A circuit has a current of 5 amperes and a voltage of 20 volts. What is the resistance of the circuit?

$$I = 5A$$

$$V = 20V$$

$$V = IR$$

$$\frac{V}{I} = R$$

$$\frac{20V}{5A} = R$$

~~$$4\Omega = R$$~~

- ⑤ A resistor dissipates power at a rate of 12 watts when a current of 2 amperes passes through it. What is the resistance of the resistor?

* $P = IV$

$$P = I^2R$$

$$I = 2A$$

$$\frac{P}{I^2} = R$$

$$P = 12$$

$$\frac{12}{4} = R$$

~~$$3\Omega = R$$~~

- ⑥ A circuit has a resistance of 8 ohms and draws a current of 3 amperes. What is the power dissipated by the circuit?

* $R = 8\Omega$

$$P = I^2R$$

$$I = 3A$$

$$= 3^2 \times 8$$

$$= 9 \times 8$$

~~$$= 72W$$~~

⑦ A power supply delivers a current of 2 amperes to a circuit with a resistance of 15 ohms. What is the power supplied by the source?

$$I = 2 \text{ A}$$

$$R = 15 \Omega$$

$$P = I^2 R$$

$$= 2^2 \times 15$$

$$= \underline{\underline{60 \text{ W}}}$$

⑧ A device operates at a power of 60 watts, and has a voltage of 120 volts. What is the current consumed by the device?

$$P = 60$$


$$V = 120 \text{ V}$$

$$P = IV$$

$$\frac{P}{V} = I$$

$$\frac{60}{120} = I$$
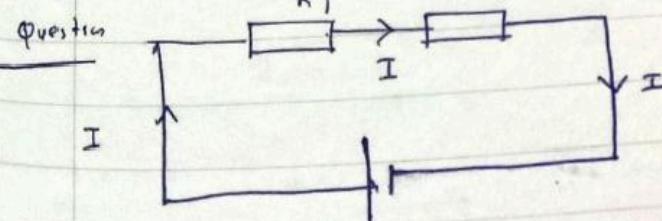
$$\underline{\underline{\frac{1}{2} \text{ A} = I}}$$



$$R = R_1 + R_2$$

$$= 6\Omega + 12\Omega$$

$$= \cancel{6\Omega} + \cancel{12\Omega}$$


$$= 18\Omega$$

$$i = 1 \text{ A}$$

$$V = IR$$

$$= 1 \times 18$$

$$= \underline{\underline{18 \text{ V}}}$$

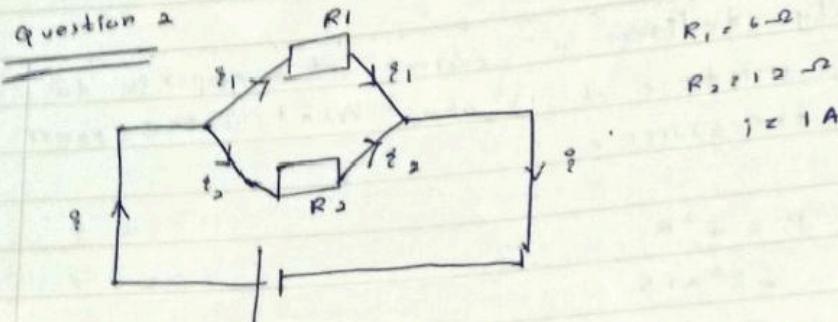Question 2

$$R_1 = 6 \Omega$$

$$R_2 = 12 \Omega$$

$$i = 1A$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{6} + \frac{1}{12}$$

$$= \frac{2+1}{12}$$

$$= \frac{3}{12}$$


$$\underline{\underline{R = 4 \Omega}}$$

$$V = IR$$

$$= 1 \times 4$$

$$= \underline{\underline{4V}}$$

①

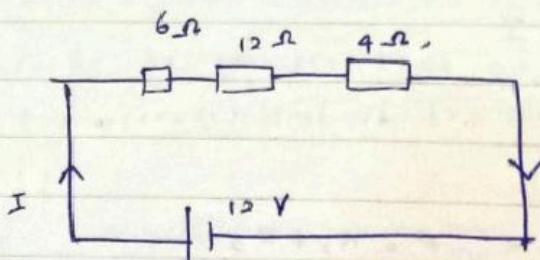
 $6 \Omega, 12 \Omega, 4 \Omega,$
 $12V$

(I)

$$R = R_1 + R_2 + R_3$$

$$= 6 + 12 + 4$$

$$= \underline{\underline{22 \Omega}}$$

②

$$V = IR$$


$$\Rightarrow \frac{V}{R} = I$$

$$\Rightarrow \frac{12V}{22 \Omega} = I$$

$$\frac{1}{22} = I$$

Probable
Ans

(i) The resistors 4Ω , 12Ω , 6Ω

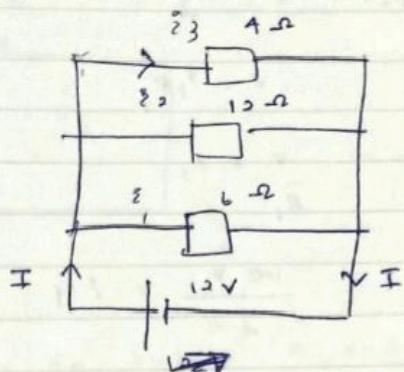

$$(i) \text{ resistance (total)} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{R}$$

$$\frac{1}{4} + \frac{1}{12} + \frac{1}{6} = \frac{1}{R}$$

$$\frac{3 + 1 + 2}{12} = \frac{1}{R}$$

$$\frac{6}{12} = \frac{1}{R}$$

$$\frac{12}{6} = R$$

$$\underline{R = 2\Omega}$$

(ii) What current is gained from the electric supply?

$$V = IR$$

$$I = \frac{V}{R} = \underline{\underline{R}}$$

$$\approx \frac{12}{2}$$

$$\underline{\underline{I = 6A}}$$

Date _____ No. _____

(iv) ~~voltage~~, current flowing through $\text{6}\Omega$.

$$V = \mathcal{E}_1 R_1$$

$$\frac{V}{R_1} = \mathcal{E}_1$$

$$\frac{12V}{6\Omega} = \mathcal{E}_1$$

$$\underline{\underline{2A = \mathcal{E}_1}}$$

(v) Current flowing through 12Ω .

$$V = \mathcal{E}_2 R_2$$

$$\frac{V}{R_2} = \mathcal{E}_2$$

$$\frac{12V}{12\Omega} = \mathcal{E}_2$$

$$\underline{\underline{1A = \mathcal{E}_2}}$$


(vi) Current flowing through 4Ω

$$V = \mathcal{E}_3 R_3$$

$$\frac{V}{R_3} = \mathcal{E}_3$$

$$\frac{12V}{4\Omega} = \mathcal{E}_3$$
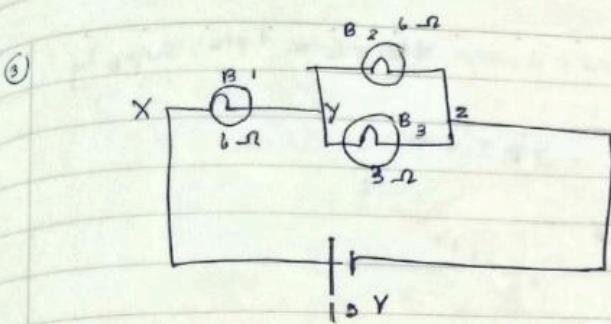
$$\underline{\underline{3A = \mathcal{E}_3}}$$



Q3 Resistors 3d

6 ohm and 3 ohm

No

- (I) total resistance the two bulbs B_2 and B_3 (between Y and Z)

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\checkmark \quad \frac{1}{6} + \frac{1}{3}$$

$$\frac{1+2}{6}$$

$$\frac{1}{R} = \frac{3}{6}$$

$$R = \underline{\underline{2\Omega}}$$


$$R = 2\Omega$$

- (II) total resistance between the two points X and Z

$$R = R_3 + R$$

$$= 6 + 2$$

$$\underline{\underline{R = 8\Omega}}$$

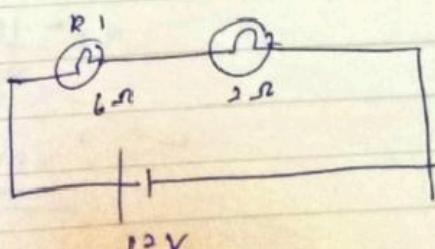

(iii)

What is the current gained from the electric supply

$$V = IR$$

$$I = \frac{V}{R}$$

12 over 8

$$I = \frac{12}{8} A = 1.5 A$$

(iv)

do potential difference between X and Y

$$V = IR$$

$$\frac{12}{8} \times 3 = 3$$

$$3V$$

(v)

Calculate the potential difference between Y and Z

$$V = IR$$

$$\frac{12}{8} \times 3 = 3$$

$$3V$$

Q1) current flowing through B_2 bulb

$$V = IR$$

$$I = \frac{V}{R}$$

$$= \frac{3}{6} =$$

$$= \frac{1}{2} A = 0.5 A$$

Q1) Current through the bulb B_3

$$I = \frac{V}{R}$$

$$I = I_1 + I_2$$

$$= \frac{9}{3} = 3$$

$$= 3 A$$

Q1) If B_3 is removed, Then what would be the current gain from the electric supply



$$R = 12 \Omega$$

$$V = IR$$

$$\frac{V}{R} = I$$

$$\frac{12V}{12\Omega} = I$$

$$1 A = I$$

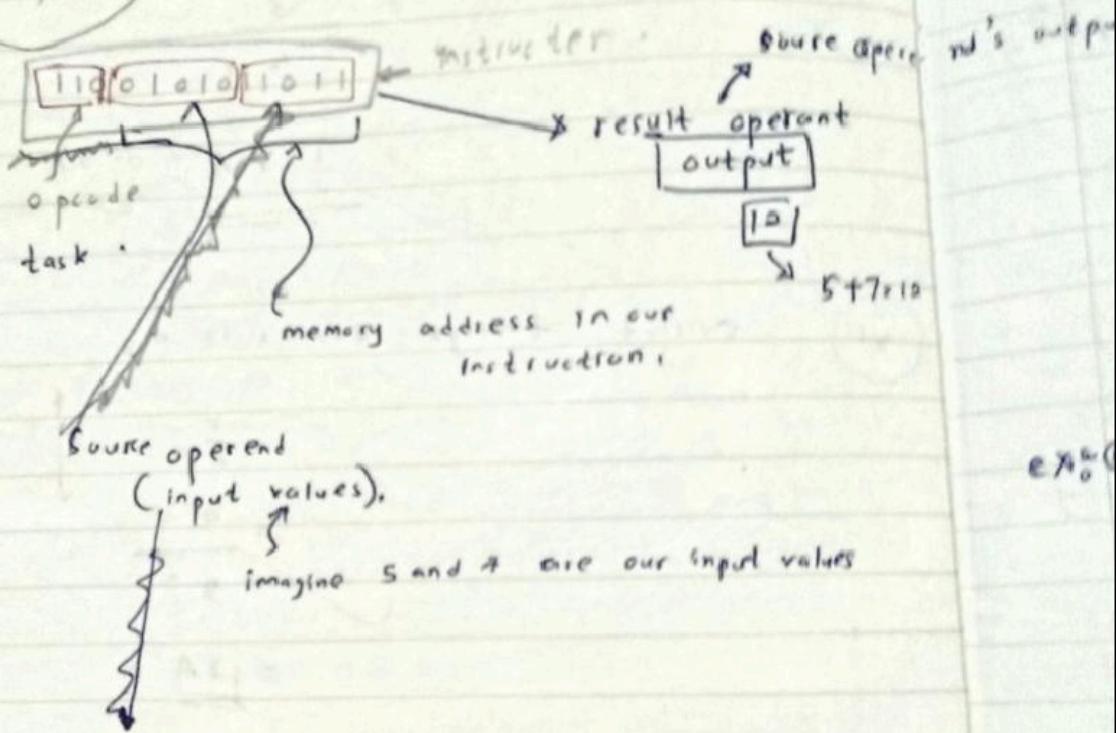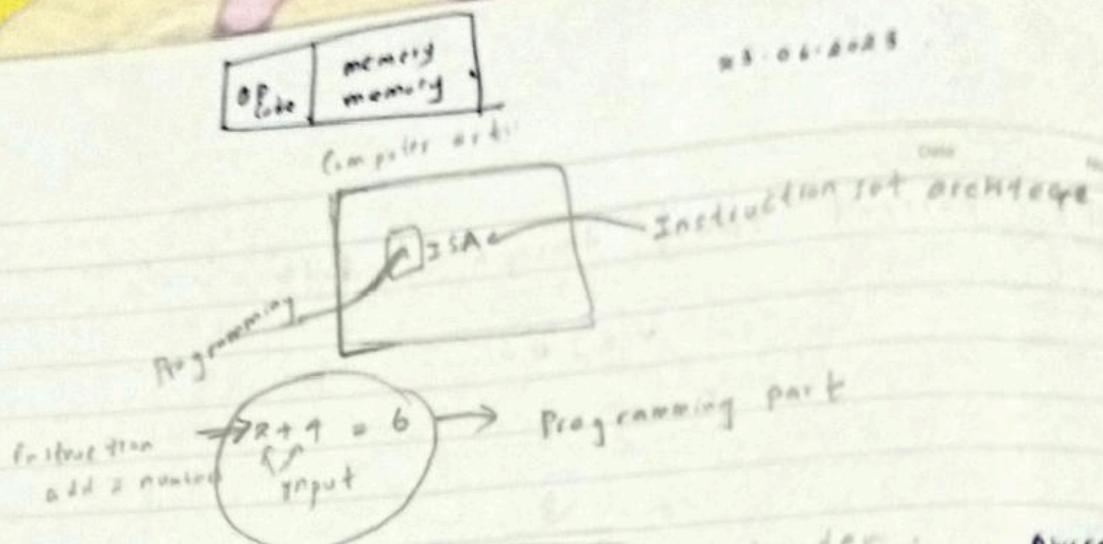

↳ instruction store ~~in~~ (register, memory)

Explicit \Rightarrow instruction do address no.

Implicit \Rightarrow processor do instruction no address and called this assumption zero no (because zero is zero).

$R_1 + R_2 = S$ result
 operator
 operand

Instruction Format

Instruction format has 3 fields



0 decimal input

ASCII value

\$50

Then convert the binary

binary 110010₂

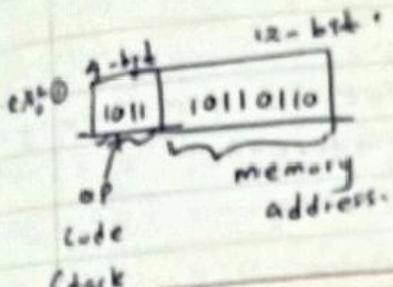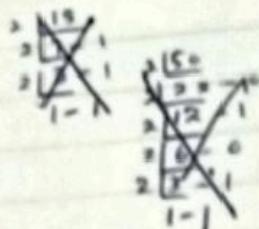

$\begin{array}{r} \$50 \\ \times 16 \\ \hline 1000 \\ 100 \\ \hline 100000 \end{array}$
 1-1

How many operations \Rightarrow (instruction).

size of op code.

$$= \underline{\underline{2^4 = 16}}$$

How many memory addresses generated by the task?


memory field size

2

$$\times 2^{12}$$

Consider a computer that is used for simple numerical problems. It uses 9 bits for an opcode, and 25 bits for a memory address.

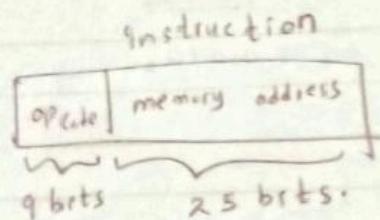- (a) What is the size of its instruction? 34 bits
- (b) How many different instructions can it have? ~~2^9 = 512~~



size of the instruction = size of the ^{op code} + size of the ^{memory address}

$$= 9 + 25$$

$$= \underline{34 \text{ bits.}}$$

- (c) What is the maximum memory size that it can address?
(Hint: Assume that $2^{10} \text{ is about } 1 \text{ M}$)

How many memory addresses = $2^{\text{size of address field}}$.




$$2^{25} = 2^{20} \times 2^5$$

$$= 1 \text{ M} \times 32$$

$$\leftarrow \underline{\underline{32 \text{ M}}}$$

instruction

Computer give a command.

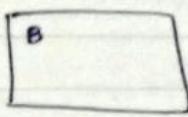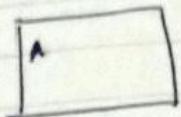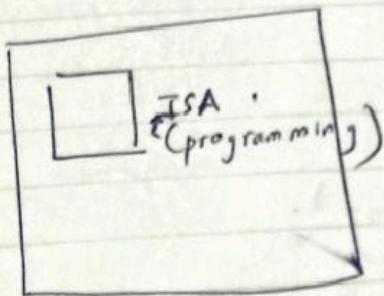instruction \Rightarrow (2) + (4) function~~to bad function~~Set of instruction \Rightarrow function.


ISA implement hardware

& data types

& Instructions


& registers

$$\varnothing \text{ num } x = 0$$

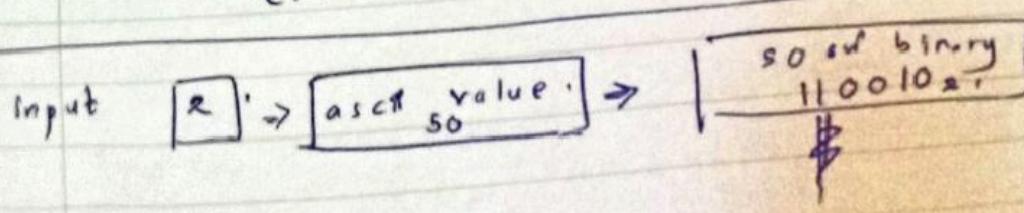
exception handling
error

$$\begin{array}{r}
 2 | 50 \\
 2 | 25 - 0 \\
 2 | 12 - 1 \\
 2 | 6 - 0 \\
 2 | 3 - 0 \\
 \hline
 1 - 1
 \end{array}$$

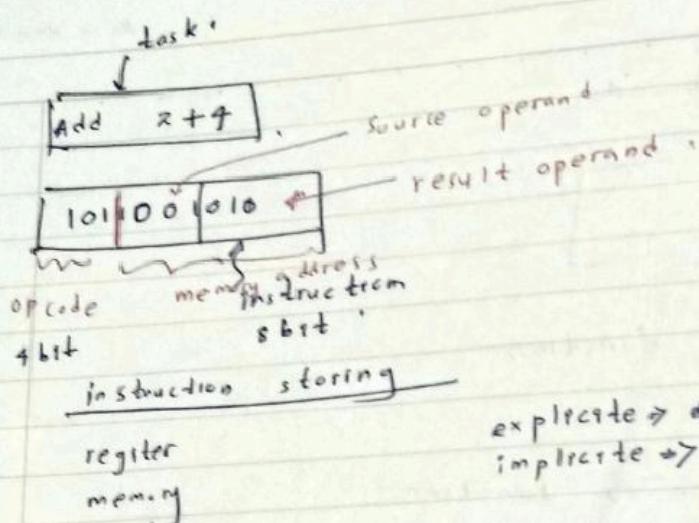result \rightarrow
 operand
 source code \rightarrow input
 opcode \rightarrow



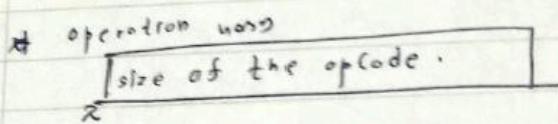explicit \Rightarrow run 8000000000000000.
 implicit \Rightarrow run 0000000000000000
 demand demultiplex word bus
 or which



$$R^f = 16 \text{ (opcode and operation word)}.$$

Memory address can a task generate

\rightarrow R⁸

\rightarrow R²⁵⁶

Instruction format

Quick Review Question 2

memory locations

Date

No

Given a CPU with a 8-bit word, 8 registers, and instructions that are exactly 1 word long and which has 2 operands.

- How long can the opcode field be in an instruction?
- How many instructions can the CPU support?




$$2^2 = 4 \text{ bits}$$

(a)



(b)

$$2^3 = 8 \text{ bits}$$

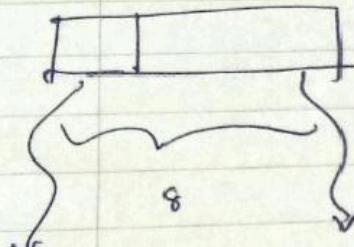

q bit

memory address on op Code and Reg. No. of bits = 4 bits

4 bit

8 bit (instruction size).

(a)

$$2^4 = 16$$

bits

* Consider a computer that is used for simple numerical problems. It uses 6 bits for an opcode, and 12 bits for a memory address.

- What is the size of its instruction? 18 bits.
- How many different instructions can it have? ~~2^6 bits~~ 2^6 bits
- What is the maximum memory size that it can address? 2^12
 Hint: Assume the 2^12 is about 4K
 ProMate